

Name: Joel Pam Pam ID# 1001428105

Date Submitted: 4/26/2026 Time Submitted 9:20 PM

CSE 3341 – Digital Logic Design II
CSE 5357 – Advanced Digital Logic Design

Spring Semester 2026

Term Project

Half-Precision Floating-Point Adder Subtractor

(100+ Points)

Due by April 28, 2026, 11:59 pm

Submit through Canvas Assignments

Requirements Summary:

This project focuses on doing half precision floating point addition and subtraction based on the IEEE 754 standards. Inputs A and B are entered in as Hex values to represent the 16 bit binary numbers and the output is also displayed as a Hex value on the hex display.

Input Requirements:

1. Input must be entered on the CSE 4 x 4 keyboard
2. Input must be entered in binary IEEE format which can be done by entering in as a HEX value. For example, 3.75 in IEEE binary format is 0100001110000000 which should be entered in as 4380 on the keyboard
3. Operand A should be entered by keying in the number and pressing key 2 on the Hex Board
4. Operand B should be entered by keying in the number and pressing key 3 on the Hex Board
5. Results R will be computed by pressing key 4 on the Hex Board
6. Key 0 on the DE10 can be used to reset

Output Requirements:

1. Operand A will be display on the Hex display in hex according to IEEE 754 half precision format
2. Operand B will be displayed on the Hex display in hex according to IEEE 754 half precision format after pressing key 3
3. Result R will be displayed on the Hex display in hex according to IEEE 754 half precision format after pressing key 4
4. LEDR0 on the DE10 will showcase the Overflow Flag
5. LEDR1 on the DE10 will showcase the Underflow Flag

Complete process to use the floating adder/subtractor on the DE10:

1. Enter operand A in hex based on the IEEE 754 half precision format and press key 2. This will display A on the Hex display
2. Enter operand B in hex based on the IEEE 754 half precision format and press key 3. This will display B on the Hex display
3. Finally the Result will be displayed on the Hex display after pressing key 4 on the hex board.

Description of any added features:


No Additional Added features

-BONUS: Early Submission

-BONUS: Subtraction

-BONUS: Overflow and Underflow Flags

Organization Diagram:

 

Test Results:

- Summary:**

A	Hex value of A	B	Hex value of B	Result (R)	Hex value of R	Overflow	Underflow
3.75	0x4380	5.125	0x4520	8.875	0x4870	0	0
3.75	0x4380	-5.125	0xC520	-1.375	0xBD80	0	0
-3.75	0xC380	5.125	0x4520	1.375	0x3D80	0	0
9.5	0x48C0	0.5625	0x3880	10.0625	0x4908	0	0
9.5	0x48C0	-0.5625	0xB880	8.9375	0x4878	0	0
-9.5	0xC8C0	-0.5625	0xB880	-10.0625	0xC908	0	0
125.125	0x57D2	-12.0625	0xCA08	113.0625	0x5711	0	0
1000	0x63D0	1049	0x6419	2050	0x6801	0	0
65504	0x7BFF	65504	0x7BFF	$+\infty$	0x7C00	1	0
-65504	0xFBFF	-65504	0xFBFF	$-\infty$	0xFC00	1	0
0.0000610948	0x0401	-0.00006103515625	0x8400	+0	0x0000	0	1
0.000244140625	0x0C00	-0.00024437904358	0x8C01	-0	0x8000	0	1

- Demonstration**

<https://youtu.be/Am9OUKdBFNQ?si=iWlaEgJJ6qxy8XxN>

SystemVerilog Code:

```
1 //Half Precision Floating Point Adder/Subtractor Top Level module - DE10 Implementaton
2 module HalfPrecisionFPAdder
3 (
4     input clk,
5     input reset,
6     input [3:0] row,
7     output [3:0] col,
8     output logic [3:0] CAT,
9     output logic [0:6] SEG,
10    input key2,key3,key4,
11    output Overflow, Underflow
12 );
13
14    logic [15:0] BCDSM,Result;
15    logic [31:0] Y;
16    logic MuxRate, CounterCLK;
17    logic [3:0] HEX0, HEX1, HEX2, HEX3;
18    logic value, trig;
19    logic [4:0] Exponent;
20    logic [9:0] Mantissa;
21    logic [15:0] A_reg, B_reg;
22
23
24    keypad_input #(DIGITS(4)) keypad_input_inst
25    (
26        .clk(clk),
27        .reset(reset),
28        .row(row),
29        .col(col),
30        .out(BCDSM),
31        .value(value),
32        .trig(trig)
33    );
34
```

```
34
35
36    ClockLadder ClockLadder_inst
37    (
38        .clock(clk) , // input clock_sig
39        .clear(reset) , // input clear_sig
40        .Y(Y) // output [31:0] Y_sig
41    );
42    assign CounterCLK = Y[22];
43    assign MuxRate = Y[17];
44
45    logic [1:0] displayse1;
46
47    always_ff @(posedge clk, negedge reset) begin
48        if(!reset) begin
49            A_reg <= 0;
50            B_reg <= 0;
51            displayse1 <= 2'b11;
52        end
53        else if(!key2) begin
54            A_reg <= BCDSM;
55            displayse1 <= 2'b00;
56        end
57        else if(!key3) begin
58            B_reg <= BCDSM;
59            displayse1 <= 2'b01;
60        end
61        else if(!key4) begin
62            displayse1 <= 2'b10;
63        end
64    end
```

```

65
66 logic [15:0] Aout, Bout;
67 logic addsub;
68 logic sign;
69 CU CU_inst
70 (
71     .A(A_reg) , // input [15:0] A_sig
72     .B(B_reg) , // input [15:0] B_sig
73     .Aout(Aout) , // output [15:0] Aout_sig
74     .Bout(Bout) , // output [15:0] Bout_sig
75     .addsub(addsub), // output addsub_sig
76     .sign(sign)
77 );
78
79 logic [4:0] ExponentSub, ExponentAdd;
80 logic [9:0] MantissaAdd, MantissaSub;
81 logic UA;
82 HPFPSubtractor HPFPSubtractor_inst
83 (
84     .A(Aout) , // input [15:0] A_sig
85     .B(Bout) , // input [15:0] B_sig
86     .Exponent(ExponentSub) , // output [4:0] Exponent_sig
87     .Mantissa(MantissaSub), // output [9:0] Mantissa_sig
88     .exponentsubtractorcout(exponentsubtractorcout)
89 );
90
91 HPFPAdder HPFPAdder_inst
92 (
93     .A(Aout) , // input [15:0] A_sig
94     .B(Bout) , // input [15:0] B_sig
95     .Exponent(ExponentAdd) , // output [4:0] Exponent_sig
96     .Mantissa(MantissaAdd) // output [9:0] Mantissa_sig
97 );
98
99 );
100 assign Exponent = addsub ? ExponentSub : ExponentAdd;
101 assign Mantissa = addsub ? MantissaSub : MantissaAdd;
102 logic OE,UE;
103 OverflowUnderflow OverflowUnderflow_inst
104 (
105     .EA(A_reg[14:10]) , // input [4:0] EA_sig
106     .EB(B_reg[14:10]) , // input [4:0] EB_sig
107     .finalmantissa(Mantissa) , // input [9:0] finalmantissa_sig
108     .finalexponent(Exponent) , // input [5:0] finalexponent_sig
109     .exponentsubtractorcout(exponentsubtractorcout) , // input exponentsubtractorcout_sig
110     .Overflow(OE) , // output Overflow_sig
111     .Underflow(UE) // output Underflow_sig
112 );
113
114 assign Overflow = addsub ? 1'b0 : OE;
115 assign Underflow = addsub ? UE : 1'b0;
116
117 logic [15:0] Resulttemp;
118
119 always_comb begin
120     if(Overflow)
121         Resulttemp = {sign,5'b11111,10'b0000000000};
122     else if (Underflow)
123         Resulttemp = {sign,5'b00000,10'b0000000000};
124     else
125         Resulttemp = {sign,Exponent,Mantissa};
126 end
127
128

```

```

127
128
129 assign Result = Resulttemp;
130 logic [15:0] display;
131
132 always_comb begin
133     case(displaysel)
134         2'b00: display = A_reg;
135         2'b01: display = B_reg;
136         2'b10: display = Result;
137         default: display = BCDSM;
138     endcase
139 end
140
141
142 assign HEX0 = display[3:0];
143 assign HEX1 = display[7:4];
144 assign HEX2 = display[11:8];
145 assign HEX3 = display[15:12];
146
147 Multi7segdisplay Multi7segdisplay_inst
148 (
149     .HEX0(HEX0), // input [3:0] HEX0_sig
150     .HEX1(HEX1), // input [3:0] HEX1_sig
151     .HEX2(HEX2), // input [3:0] HEX2_sig
152     .HEX3(HEX3), // input [3:0] HEX3_sig
153     .CLK(MuxRate), // input CLK_sig
154     .Reset(reset), // input Reset_sig
155     .Load(CounterCLK), // input Load_sig
156     .SEG(SEG), // output [0:6] SEG_sig
157     .CAT(CAT) // output [3:0] CAT_sig
158 );
159
160 endmodule

```

```

1 //Control Module to decide addition or Subtraction based on the sign bit
2 module CU
3 (
4     input [15:0] A,B,
5     output [15:0] Aout, Bout,
6     output addsub,
7     output sign
8 );
9 assign addsub = A[15] ^ B[15];
10
11 always_comb begin
12     if(addsub) begin
13         if(A[14:0] > B[14:0]) begin
14             Aout = A;
15             Bout = B;
16             sign = A[15];
17         end
18         else begin
19             Aout = B;
20             Bout = A;
21             sign = B[15];
22         end
23     end
24     else begin
25         Aout = A;
26         Bout = B;
27         sign = A[15];
28     end
29 end
30
31 endmodule

```



```

1 //Clock Ladder
2 module ClockLadder
3 (
4     input clock, clear,
5     output logic [31:0] Y
6 );
7     always_ff @ (posedge clock, negedge clear)
8         if(~clear) Y <= 1'b0;
9         else Y <= Y + 1'b1;
10 endmodule
11

```

```

1 //OverFlow and UnderFlow Flag module
2 module OverflowUnderflow
3 (
4     input [4:0] EA, EB,
5     input [9:0] finalmantissa,
6     input [5:0] finalexponent,
7     input exponentsubtractorcout,
8     output Overflow, Underflow
9 );
10     logic Exception;
11     logic zero;
12     assign Exception = (&EA) | (&EB);
13     assign zero = Exception ? 1'b0 : (finalmantissa == 10'd0) ? 1'b1 : 1'b0;
14     assign Overflow = (finalexponent > 5'b11110) && !zero;
15     assign Underflow = ~exponentsubtractorcout;
16
17 endmodule

```

```

1 //Half Precision Floating Point Adder
2 module HPFPAdder
3 (
4     input [15:0] A,B,
5     output [4:0] Exponent,
6     output [9:0] Mantissa
7 );
8
9     logic [4:0] modexpsubout, expoincmuxout;
10    logic modexpocout;
11    logic [9:0] smuxout, amuxout;
12    logic [10:0] shiftermuxout, mantissarsout, addermuxout;
13    logic [10:0] adderout;
14    logic addercout;
15
16
17    ModularExponentSub #(N(5)) ModularExponentSub_inst
18    (
19        .A(B[14:10]), // input [(N-1):0] A_sig
20        .B(A[14:10]), // input [(N-1):0] B_sig
21        .out(modexpsubout), // output [(N-1):0] out_sig
22        .cout(modexpocout) // output cout_sig
23    );
24
25    tenbitmux tenbitmux_shiftermux
26    (
27        .A(A[9:0]), // input [9:0] A_sig
28        .B(B[9:0]), // input [9:0] B_sig
29        .select(modexpocout), // input select_sig
30        .out(smuxout) // output [9:0] out_sig
31    );

```

```

31 );
32 assign shiftermuxout = {1'b1,smuxout};
33
34 tenbitmux tenbitmux_addermux
35 (
36     .A(B[9:0]) , // input [9:0] A_sig
37     .B(A[9:0]) , // input [9:0] B_sig
38     .select(modexpocout) , // input select_sig
39     .out(amuxout) // output [9:0] out_sig
40 );
41 assign addermuxout = {1'b1,amuxout};
42
43
44 fivebitmux expoincmux
45 (
46     .A(B[14:10]) , // input [4:0] A_sig
47     .B(A[14:10]) , // input [4:0] B_sig
48     .select(modexpocout) , // input select_sig
49     .out(expoincmuxout) // output [4:0] out_sig
50 );
51
52 BarrelShifter MantissaRightShifter
53 (
54     .A(shiftermuxout) , // input [10:0] A_sig
55     .B(modexpocout) , // input [4:0] B_sig
56     .Y(mantissarsout) // output [10:0] Y_sig
57 );
58
59
60 CSA CSA_inst
61 (
62     .A(mantissarsout) , // input [10:0] A_sig
63     .B(addermuxout) , // input [10:0] B_sig
64     .Cin(1'b0) , // input Cin_sig
65     .Sum(addercout) , // output [10:0] Sum_sig
66     .Cout(addercout) // output Cout_sig
67 );
68
69 logic select;
70
71 always_comb begin
72     if(addercout)
73         select = 1'b1;
74     else
75         select = 1'b0;
76 end
77
78 ControlledExponent_INC_DEC ControlledExponent_INC_DEC_inst
79 (
80     .A(expoincmuxout) , // input [4:0] A_sig
81     .select(select) , // input select_sig
82     .cin(~addercout) , // input cin_sig
83     .exponent(Exponent) // output [4:0] exponent_sig
84 );
85
86
87 MantissaNormalizer MantissaNormalizer_inst
88 (
89     .A(addercout) , // input [10:0] A_sig
90     .select(addercout) , // input select_sig
91     .mantissa(Mantissa) // output [9:0] mantissa_sig
92 );
93
94 endmodule
95

```

```

1  //Carry Select Adder
2  module CSA
3  (
4      input [10:0] A,B,
5      input Cin,
6      output [10:0] Sum,
7      output Cout
8  );
9
10
11     wire [4:0] lower;
12     wire [5:0] RCA2, RCA3, upper;
13     wire C80, C81, C4;
14
15     ParameterizedRCA #(N(5)) ParameterizedRCA_inst0
16     (
17         .Cin(Cin), // input Cin_sig
18         .A(A[4:0]), // input [(N-1):0] A_sig
19         .B(B[4:0]), // input [(N-1):0] B_sig
20         .Sum(lower[4:0]), // output [(N-1):0] Sum_sig
21         .Cout(C4) // output Cout_sig
22     );
23
24     ParameterizedRCA #(N(6)) ParameterizedRCA_inst1
25     (
26         .Cin(1'b0), // input Cin_sig
27         .A(A[10:5]), // input [(N-1):0] A_sig
28         .B(B[10:5]), // input [(N-1):0] B_sig
29         .Sum(RCA2), // output [(N-1):0] Sum_sig
30         .Cout(C80) // output Cout_sig
31     );
32
33
34     ParameterizedRCA #(N(6)) ParameterizedRCA_inst2
35     (
36         .Cin(1'b1), // input Cin_sig
37         .A(A[10:5]), // input [(N-1):0] A_sig
38         .B(B[10:5]), // input [(N-1):0] B_sig
39         .Sum(RCA3), // output [(N-1):0] Sum_sig
40         .Cout(C81) // output Cout_sig
41     );
42
43     Mux R5_inst
44     (
45         .A(RCA3[0]), // input A_sig
46         .B(RCA2[0]), // input B_sig
47         .S(C4), // input C4_sig
48         .Out(upper[0]) // output R_sig
49     );
50
51     Mux R6_inst
52     (
53         .A(RCA3[1]), // input A_sig
54         .B(RCA2[1]), // input B_sig
55         .S(C4), // input C4_sig
56         .Out(upper[1]) // output R_sig
57     );

```

```

58     Mux R7_inst
59     (
60         .A(RCA3[2]) , // input A_sig
61         .B(RCA2[2]) , // input B_sig
62         .S(C4) , // input C4_sig
63         .Out(upper[2]) // output R_sig
64     );
65
66     Mux R8_inst
67     (
68         .A(RCA3[3]) , // input A_sig
69         .B(RCA2[3]) , // input B_sig
70         .S(C4) , // input C4_sig
71         .Out(upper[3]) // output R_sig
72     );
73
74     Mux R9_inst
75     (
76         .A(RCA3[4]) , // input A_sig
77         .B(RCA2[4]) , // input B_sig
78         .S(C4) , // input C4_sig
79         .Out(upper[4]) // output R_sig
80     );
81
82     Mux R10_inst
83     (
84         .A(RCA3[5]) , // input A_sig
85         .B(RCA2[5]) , // input B_sig
86         .S(C4) , // input C4_sig
87         .Out(upper[5]) // output R_sig
88     );

```

```

82     Mux R10_inst
83     (
84         .A(RCA3[5]) , // input A_sig
85         .B(RCA2[5]) , // input B_sig
86         .S(C4) , // input C4_sig
87         .Out(upper[5]) // output R_sig
88     );
89
90     Mux Cout_inst
91     (
92         .A(C81) , // input A_sig
93         .B(C80) , // input B_sig
94         .S(C4) , // input C4_sig
95         .Out(Cout) // output R_sig
96     );
97
98     assign Sum = {upper,lower};
99 endmodule

```

```

1 //Mux
2 module Mux(
3
4     input A,
5     input B,
6     input S,
7     output Out
8 );
9
10     assign Out = S ? A : B;
11
12 endmodule
13

```

```

1 //Parameterized Ripple Carry Adder
2 module ParameterizedRCA #(parameter N = 8)
3 (
4     input Cin,
5     input [N-1:0] A,B,
6     output [N-1:0] Sum,
7     output Cout
8 );
9
10 wire [N:0] C;
11 assign C[0] = Cin;
12 assign Cout = C[N];
13
14 genvar i;
15 generate
16     for(i=0;i<N;i=i+1)
17     begin:full_adder
18         FullAdder FullAdder_inst (A[i],B[i],C[i],Sum[i],C[i+1]);
19     end
20 endgenerate
21
22 endmodule
23

```

```

1 //FullAdder
2 module FullAdder(
3     input ai,bi, cini,
4     output logic si,couti);
5     always_comb
6     case({ai,bi,cini})
7         3'b000: begin couti = 1'b0; si = 1'b0; end
8         3'b001: begin couti = 1'b0; si = 1'b1; end
9         3'b010: begin couti = 1'b0; si = 1'b1; end
10        3'b011: begin couti = 1'b1; si = 1'b0; end
11        3'b100: begin couti = 1'b0; si = 1'b1; end
12        3'b101: begin couti = 1'b1; si = 1'b0; end
13        3'b110: begin couti = 1'b1; si = 1'b0; end
14        3'b111: begin couti = 1'b1; si = 1'b1; end
15    endcase
16 endmodule
17

```

```

1 //Controlled Exponent Increment and Decrement(Top Level)
2 module ControlledExponent_INC_DEC
3 (
4     input [4:0] A,
5     input select,cin,
6     output [4:0] exponent
7 );
8
9     logic [5:0] C;
10    assign C[0] = cin;
11
12    FullAdder FullAdder_instS0(.ai(A[0]) ,.bi(select ^ cin) ,.cini(C[0]) ,.si(exponent[0]) ,.couti(C[1]));
13    FullAdder FullAdder_instS1(.ai(A[1]) ,.bi(cin ^ 1'b0) ,.cini(C[1]) ,.si(exponent[1]) ,.couti(C[2]));
14    FullAdder FullAdder_instS2(.ai(A[2]) ,.bi(cin ^ 1'b0) ,.cini(C[2]) ,.si(exponent[2]) ,.couti(C[3]));
15    FullAdder FullAdder_instS3(.ai(A[3]) ,.bi(cin ^ 1'b0) ,.cini(C[3]) ,.si(exponent[3]) ,.couti(C[4]));
16    FullAdder FullAdder_instS4(.ai(A[4]) ,.bi(cin ^ 1'b0) ,.cini(C[4]) ,.si(exponent[4]) ,.couti(C[5]));
17
18 endmodule

```

```

1 //Mantissa Normalizer
2 module MantissaNormalizer
3 (
4     input [10:0] A,
5     input select,
6     output [9:0] mantissa
7 );
8
9     logic [10:0] U;
10    logic [9:0] Y;
11    Mux Mux_inst0(.A(A[1]), .B(A[0]), .S(select), .Out(U[0]));
12    Mux Mux_inst1(.A(A[2]), .B(A[1]), .S(select), .Out(U[1]));
13    Mux Mux_inst2(.A(A[3]), .B(A[2]), .S(select), .Out(U[2]));
14    Mux Mux_inst3(.A(A[4]), .B(A[3]), .S(select), .Out(U[3]));
15    Mux Mux_inst4(.A(A[5]), .B(A[4]), .S(select), .Out(U[4]));
16    Mux Mux_inst5(.A(A[6]), .B(A[5]), .S(select), .Out(U[5]));
17    Mux Mux_inst6(.A(A[7]), .B(A[6]), .S(select), .Out(U[6]));
18    Mux Mux_inst7(.A(A[8]), .B(A[7]), .S(select), .Out(U[7]));
19    Mux Mux_inst8(.A(A[9]), .B(A[8]), .S(select), .Out(U[8]));
20    Mux Mux_inst9(.A(A[10]), .B(A[9]), .S(select), .Out(U[9]));
21    Mux Mux_instA(.A(1'b0), .B(A[10]), .S(select), .Out(U[10]));
22
23    always_comb begin
24        if(select == 1) begin
25            if(A[0] == 1) begin
26                Y = U[9:0] + 1'b1;
27            end
28            else begin
29                Y = U[9:0];
30            end
31        end
32        else begin
33            Y = A[9:0];
34        end
35    end
36
37    assign mantissa = Y;
38
39 endmodule

```

```

1 //Right Barrel Shifter
2 module BarrelShifter (
3
4     input [10:0] A,
5     input [4:0] B,
6     output [10:0] Y
7 );
8
9
10    logic [10:0] V,U,W,X;
11
12    //B4
13    Mux Mux_inst0(.A(1'b0), .B(A[0]), .S(B[4]), .Out(U[0]));
14    Mux Mux_inst1(.A(1'b0), .B(A[1]), .S(B[4]), .Out(U[1]));
15    Mux Mux_inst2(.A(1'b0), .B(A[2]), .S(B[4]), .Out(U[2]));
16    Mux Mux_inst3(.A(1'b0), .B(A[3]), .S(B[4]), .Out(U[3]));
17    Mux Mux_inst4(.A(1'b0), .B(A[4]), .S(B[4]), .Out(U[4]));
18    Mux Mux_inst5(.A(1'b0), .B(A[5]), .S(B[4]), .Out(U[5]));
19    Mux Mux_inst6(.A(1'b0), .B(A[6]), .S(B[4]), .Out(U[6]));
20    Mux Mux_inst7(.A(1'b0), .B(A[7]), .S(B[4]), .Out(U[7]));
21    Mux Mux_inst8(.A(1'b0), .B(A[8]), .S(B[4]), .Out(U[8]));
22    Mux Mux_inst9(.A(1'b0), .B(A[9]), .S(B[4]), .Out(U[9]));
23    Mux Mux_instA(.A(1'b0), .B(A[10]), .S(B[4]), .Out(U[10]));
24

```

```

24
25 //B3
26 Mux Mux_instB(.A(U[8]), .B(U[0]), .S(B[3]), .Out(V[0]));
27 Mux Mux_instC(.A(U[9]), .B(U[1]), .S(B[3]), .Out(V[1]));
28 Mux Mux_instD(.A(U[10]), .B(U[2]), .S(B[3]), .Out(V[2]));
29 Mux Mux_instE(.A(1'b0), .B(U[3]), .S(B[3]), .Out(V[3]));
30 Mux Mux_instF(.A(1'b0), .B(U[4]), .S(B[3]), .Out(V[4]));
31 Mux Mux_inst00(.A(1'b0), .B(U[5]), .S(B[3]), .Out(V[5]));
32 Mux Mux_inst01(.A(1'b0), .B(U[6]), .S(B[3]), .Out(V[6]));
33 Mux Mux_inst02(.A(1'b0), .B(U[7]), .S(B[3]), .Out(V[7]));
34 Mux Mux_inst03(.A(1'b0), .B(U[8]), .S(B[3]), .Out(V[8]));
35 Mux Mux_inst04(.A(1'b0), .B(U[9]), .S(B[3]), .Out(V[9]));
36 Mux Mux_inst05(.A(1'b0), .B(U[10]), .S(B[3]), .Out(V[10]));
37
38 //B2
39 Mux Mux_inst06(.A(V[4]), .B(V[0]), .S(B[2]), .Out(W[0]));
40 Mux Mux_inst07(.A(V[5]), .B(V[1]), .S(B[2]), .Out(W[1]));
41 Mux Mux_inst08(.A(V[6]), .B(V[2]), .S(B[2]), .Out(W[2]));
42 Mux Mux_inst09(.A(V[7]), .B(V[3]), .S(B[2]), .Out(W[3]));
43 Mux Mux_inst0A(.A(V[8]), .B(V[4]), .S(B[2]), .Out(W[4]));
44 Mux Mux_inst0B(.A(V[9]), .B(V[5]), .S(B[2]), .Out(W[5]));
45 Mux Mux_inst0C(.A(V[10]), .B(V[6]), .S(B[2]), .Out(W[6]));
46 Mux Mux_inst0D(.A(1'b0), .B(V[7]), .S(B[2]), .Out(W[7]));
47 Mux Mux_inst0E(.A(1'b0), .B(V[8]), .S(B[2]), .Out(W[8]));
48 Mux Mux_inst0F(.A(1'b0), .B(V[9]), .S(B[2]), .Out(W[9]));
49 Mux Mux_inst10(.A(1'b0), .B(V[10]), .S(B[2]), .Out(W[10]));
50
51 //B1
52 Mux Mux_inst11(.A(W[2]), .B(W[0]), .S(B[1]), .Out(X[0]));
53 Mux Mux_inst12(.A(W[3]), .B(W[1]), .S(B[1]), .Out(X[1]));
54 Mux Mux_inst13(.A(W[4]), .B(W[2]), .S(B[1]), .Out(X[2]));
55 Mux Mux_inst14(.A(W[5]), .B(W[3]), .S(B[1]), .Out(X[3]));
56 Mux Mux_inst15(.A(W[6]), .B(W[4]), .S(B[1]), .Out(X[4]));
57 Mux Mux_inst16(.A(W[7]), .B(W[5]), .S(B[1]), .Out(X[5]));
58 Mux Mux_inst17(.A(W[8]), .B(W[6]), .S(B[1]), .Out(X[6]));
59 Mux Mux_inst18(.A(W[9]), .B(W[7]), .S(B[1]), .Out(X[7]));
60 Mux Mux_inst19(.A(W[10]), .B(W[8]), .S(B[1]), .Out(X[8]));
61 Mux Mux_inst1A(.A(1'b0), .B(W[9]), .S(B[1]), .Out(X[9]));
62 Mux Mux_inst1B(.A(1'b0), .B(W[10]), .S(B[1]), .Out(X[10]));
63
64 //B0
65 Mux Mux_inst1C(.A(X[1]), .B(X[0]), .S(B[0]), .Out(Y[0]));
66 Mux Mux_inst1D(.A(X[2]), .B(X[1]), .S(B[0]), .Out(Y[1]));
67 Mux Mux_inst1E(.A(X[3]), .B(X[2]), .S(B[0]), .Out(Y[2]));
68 Mux Mux_inst1F(.A(X[4]), .B(X[3]), .S(B[0]), .Out(Y[3]));
69 Mux Mux_inst100(.A(X[5]), .B(X[4]), .S(B[0]), .Out(Y[4]));
70 Mux Mux_inst101(.A(X[6]), .B(X[5]), .S(B[0]), .Out(Y[5]));
71 Mux Mux_inst102(.A(X[7]), .B(X[6]), .S(B[0]), .Out(Y[6]));
72 Mux Mux_inst103(.A(X[8]), .B(X[7]), .S(B[0]), .Out(Y[7]));
73 Mux Mux_inst104(.A(X[9]), .B(X[8]), .S(B[0]), .Out(Y[8]));
74 Mux Mux_inst105(.A(X[10]), .B(X[9]), .S(B[0]), .Out(Y[9]));
75 Mux Mux_inst106(.A(1'b0), .B(X[10]), .S(B[0]), .Out(Y[10]));
76
77 endmodule

```



```

1 //Modular Exponent Subtractor(Top Level)
2 module ModularExponentSub #(parameter N = 8)
3 (
4     input [N-1:0] A, B,
5     output [N-1:0] out,
6     output cout
7 );
8
9     logic [N-1:0] R,Rcomp;
10    logic Cout;
11
12    RippleCarrySub #(.N(N)) RippleCarrySub_inst
13    (
14        .A(A) , // input [(N-1):0] A_sig
15        .B(B^N{1'b1}) , // input [(N-1):0] B_sig
16        .cin(1'b1) ,
17        .R(R) , // output [(N-1):0] R_sig
18        .Cout(cout) // output Cout_sig
19    );
20    TwosCompConverter #(.N(N)) TwosCompConverter_inst
21    (
22        .A(R) , // input [(N-1):0] A_sig
23        .B(Rcomp) // output [(N-1):0] B_sig
24    );
25    twotoonemux #(.N(N))twotoonemux_inst
26    (
27        .A(R) , // input [(N-1):0] A_sig
28        .B(Rcomp) , // input [(N-1):0] B_sig
29        .select(cout) , // input select_sig
30        .out(out) // output [(N-1):0] out_sig
31    );
32
33 endmodule

```

```

1 //Ripple Carry Subtractor
2 module RippleCarrySub #(parameter N = 8)
3 (
4     input [N-1:0] A, B,
5     input cin,
6     output [N-1:0] R,
7     output Cout
8 );
9
10    logic [N:0] C;
11    assign C[0] = cin;
12    assign Cout = C[N];
13
14    genvar i;
15    generate
16        for(i=0;i<N;i=i+1)
17        begin:full_adder
18            FullAdder FullAdder_inst (A[i],B[i],C[i],R[i],C[i+1]);
19        end
20    endgenerate
21
22 endmodule

```



```

1 //Twos comp converter
2 module TwosCompConverter #(parameter N = 8)
3 (
4     input[N-1:0]A,
5     output[N-1:0]B
6 );
7     wire [N:0] ha;
8     assign ha[0] = 1'b1;
9     genvar i;
10    generate
11        for(i=0;i<N;i=i+1)
12            begin: twosFor
13                halfADDER halfADDER_inst1
14                (
15                    .s(B[i]),
16                    .cout(ha[i+1]),
17                    .a((A[i])^(1'b1)),
18                    .b(ha[i])
19                );
20            end
21        endgenerate
22    endmodule
23

```

```

1 //Half Adder
2 module halfADDER(s,cout,a,b);
3     input a,b;
4     output s, cout;
5     and(cout,a,b);
6     xor(s,a,b);
7 endmodule
8

```

```

1 //Two to one mux
2 module twotoonemux #(parameter N = 8)
3 (
4     input [N-1:0] A, B,
5     input select,
6     output [N-1:0] out
7 );
8
9     always_comb begin
10         if(select)
11             out = A;
12         else
13             out = B;
14         end
15     endmodule
16

```

```

1 //5 bit mux
2 module fivebitmux
3 (
4     input [4:0] A,B,
5     input select,
6     output [4:0] out
7 );
8
9     assign out = select ? A : B;
10
11 endmodule
12

```

```

1 //10 bit mux
2 module tenbitmux
3 (
4     input [9:0] A,B,
5     input select,
6     output [9:0] out
7 );
8
9     assign out = select ? A : B;
10
11 endmodule
12

```

```

1 //Half precision Floating Point Subtractor|
2 module HPFPSubtractor
3 (
4     input [15:0] A,B,
5     output [4:0] Exponent,
6     output [9:0] Mantissa,
7     output exponentsubtractorcout
8 );
9
10     logic [4:0] modexpesubout, expoincmuxout;
11     logic modexpocout;
12     logic [9:0] smuxout, amuxout;
13     logic [10:0] shiftermuxout, mantissarsout, addermuxout;
14     logic [10:0] adderout;
15     logic addercout;
16
17
18     ModularExponentSub #(N(5)) ModularExponentSub_inst
19     (
20         .A(A[14:10]) , // input [(N-1):0] A_sig
21         .B(B[14:10]) , // input [(N-1):0] B_sig
22         .out(modexpesubout) , // output [(N-1):0] out_sig
23         .cout(modexpocout) // output cout_sig
24     );
25
26     tenbitmux tenbitmux_shiftermux
27     (
28         .A(B[9:0]) , // input [9:0] A_sig
29         .B(A[9:0]) , // input [9:0] B_sig
30         .select(modexpocout) , // input select_sig
31         .out(smuxout) // output [9:0] out_sig
32     );
33     assign shiftermuxout = {1'b1,smuxout};
34

```

```

34
35 tenbitmux tenbitmux_addermux
36 (
37     .A(A[9:0]) , // input [9:0] A_sig
38     .B(B[9:0]) , // input [9:0] B_sig
39     .select(modexpocout) , // input select_sig
40     .out(amuxout) // output [9:0] out_sig
41 );
42 assign addermuxout = {1'b1,amuxout};
43
44
45 fivebitmux expoincmux
46 (
47     .A(A[14:10]) , // input [4:0] A_sig
48     .B(B[14:10]) , // input [4:0] B_sig
49     .select(modexpocout) , // input select_sig
50     .out(expoincmuxout) // output [4:0] out_sig
51 );
52
53 BarrelShifter MantissaRightShifter
54 (
55     .A(shiftermuxout) , // input [10:0] A_sig
56     .B(modexposubout) , // input [4:0] B_sig
57     .Y(mantissarsout) // output [10:0] Y_sig
58 );
59
60 Subtractor Subtractor_inst
61 (
62     .A(addermuxout) , // input [10:0] A_sig
63     .B(mantissarsout) , // input [10:0] B_sig
64     .cin(1'b1) , // input cin_sig
65     .cout(adderout) , // output cout_sig
66     .R(adderout) // output [10:0] R_sig
67 );
68
69 logic [3:0] leadingzeros;
70
71 always_comb begin
72     leadingzeros = 4'd11;
73     for (integer i = 10; i >= 0; i = i - 1) begin
74         if (adderout[i] && leadingzeros == 4'd11) begin
75             leadingzeros = 4'd11 - (i+1'b1);
76         end
77     end
78 end
79 ExponentSubtractor ExponentSubtractor_inst
80 (
81     .A(expoincmuxout) , // input [4:0] A_sig
82     .B(leadingzeros) , // input [3:0] B_sig
83     .exponent(Exponent) , // output [4:0] exponent_sig
84     .cout(exponentsubtractorcout)
85 );
86
87 BarrelShifterLeft MantissaNormalizerLeft_inst
88 (
89     .A(adderout) , // input [10:0] A_sig
90     .B(leadingzeros) , // input [4:0] B_sig
91     .Y(Mantissa) // output [10:0] Y_sig
92 );
93
94 endmodule

```

```

1 //Exponent Decrementer
2 module ExponentSubtractor
3 (
4     input [4:0] A,
5     input [3:0] B,
6     output [4:0] exponent,
7     output cout
8 );
9
10
11     logic [5:0] C;
12     assign C[0] = 1'b1;
13
14     FullAdder FullAdder_inst0(.ai(A[0]), .bi(B[0] ^ 1'b1), .cini(C[0]), .si(exponent[0]), .couti(C[1]));
15     FullAdder FullAdder_inst1(.ai(A[1]), .bi(B[1] ^ 1'b1), .cini(C[1]), .si(exponent[1]), .couti(C[2]));
16     FullAdder FullAdder_inst2(.ai(A[2]), .bi(B[2] ^ 1'b1), .cini(C[2]), .si(exponent[2]), .couti(C[3]));
17     FullAdder FullAdder_inst3(.ai(A[3]), .bi(B[3] ^ 1'b1), .cini(C[3]), .si(exponent[3]), .couti(C[4]));
18     FullAdder FullAdder_inst4(.ai(A[4]), .bi(1'b1), .cini(C[4]), .si(exponent[4]), .couti(C[5]));
19     assign cout = C[5];
20
21 endmodule

```

```

1 //Left Barrel Shifter
2 module BarrelShifterLeft (
3
4     input [10:0] A,
5     input [4:0] B,
6     output [9:0] Y
7 );
8
9
10     logic [10:0] V,U,W,X,T;
11
12     //B4
13     Mux Mux_inst0(.A(1'b0), .B(A[0]), .S(B[4]), .Out(U[0]));
14     Mux Mux_inst1(.A(1'b0), .B(A[1]), .S(B[4]), .Out(U[1]));
15     Mux Mux_inst2(.A(1'b0), .B(A[2]), .S(B[4]), .Out(U[2]));
16     Mux Mux_inst3(.A(1'b0), .B(A[3]), .S(B[4]), .Out(U[3]));
17     Mux Mux_inst4(.A(1'b0), .B(A[4]), .S(B[4]), .Out(U[4]));
18     Mux Mux_inst5(.A(1'b0), .B(A[5]), .S(B[4]), .Out(U[5]));
19     Mux Mux_inst6(.A(1'b0), .B(A[6]), .S(B[4]), .Out(U[6]));
20     Mux Mux_inst7(.A(1'b0), .B(A[7]), .S(B[4]), .Out(U[7]));
21     Mux Mux_inst8(.A(1'b0), .B(A[8]), .S(B[4]), .Out(U[8]));
22     Mux Mux_inst9(.A(1'b0), .B(A[9]), .S(B[4]), .Out(U[9]));
23     Mux Mux_instA(.A(1'b0), .B(A[10]), .S(B[4]), .Out(U[10]));
24
25     //B3
26     Mux Mux_instB(.A(1'b0), .B(U[0]), .S(B[3]), .Out(V[0]));
27     Mux Mux_instC(.A(1'b0), .B(U[1]), .S(B[3]), .Out(V[1]));
28     Mux Mux_instD(.A(1'b0), .B(U[2]), .S(B[3]), .Out(V[2]));
29     Mux Mux_instE(.A(1'b0), .B(U[3]), .S(B[3]), .Out(V[3]));
30     Mux Mux_instF(.A(1'b0), .B(U[4]), .S(B[3]), .Out(V[4]));
31     Mux Mux_inst00(.A(1'b0), .B(U[5]), .S(B[3]), .Out(V[5]));
32     Mux Mux_inst01(.A(1'b0), .B(U[6]), .S(B[3]), .Out(V[6]));
33     Mux Mux_inst02(.A(1'b0), .B(U[7]), .S(B[3]), .Out(V[7]));
34     Mux Mux_inst03(.A(U[0]), .B(U[8]), .S(B[3]), .Out(V[8]));
35     Mux Mux_inst04(.A(U[1]), .B(U[9]), .S(B[3]), .Out(V[9]));
36     Mux Mux_inst05(.A(U[2]), .B(U[10]), .S(B[3]), .Out(V[10]));
37

```

```

37
38 //B2
39 Mux Mux_inst06(.A(1'b0) ,.B(V[0]) ,.S(B[2]) ,.Out(W[0]));
40 Mux Mux_inst07(.A(1'b0) ,.B(V[1]) ,.S(B[2]) ,.Out(W[1]));
41 Mux Mux_inst08(.A(1'b0) ,.B(V[2]) ,.S(B[2]) ,.Out(W[2]));
42 Mux Mux_inst09(.A(1'b0) ,.B(V[3]) ,.S(B[2]) ,.Out(W[3]));
43 Mux Mux_inst0A(.A(V[0]) ,.B(V[4]) ,.S(B[2]) ,.Out(W[4]));
44 Mux Mux_inst0B(.A(V[1]) ,.B(V[5]) ,.S(B[2]) ,.Out(W[5]));
45 Mux Mux_inst0C(.A(V[2]) ,.B(V[6]) ,.S(B[2]) ,.Out(W[6]));
46 Mux Mux_inst0D(.A(V[3]) ,.B(V[7]) ,.S(B[2]) ,.Out(W[7]));
47 Mux Mux_inst0E(.A(V[4]) ,.B(V[8]) ,.S(B[2]) ,.Out(W[8]));
48 Mux Mux_inst0F(.A(V[5]) ,.B(V[9]) ,.S(B[2]) ,.Out(W[9]));
49 Mux Mux_inst10(.A(V[6]) ,.B(V[10]) ,.S(B[2]) ,.Out(W[10]));
50
51 //B1
52 Mux Mux_inst11(.A(1'b0) ,.B(W[0]) ,.S(B[1]) ,.Out(X[0]));
53 Mux Mux_inst12(.A(1'b0) ,.B(W[1]) ,.S(B[1]) ,.Out(X[1]));
54 Mux Mux_inst13(.A(W[0]) ,.B(W[2]) ,.S(B[1]) ,.Out(X[2]));
55 Mux Mux_inst14(.A(W[1]) ,.B(W[3]) ,.S(B[1]) ,.Out(X[3]));
56 Mux Mux_inst15(.A(W[2]) ,.B(W[4]) ,.S(B[1]) ,.Out(X[4]));
57 Mux Mux_inst16(.A(W[3]) ,.B(W[5]) ,.S(B[1]) ,.Out(X[5]));
58 Mux Mux_inst17(.A(W[4]) ,.B(W[6]) ,.S(B[1]) ,.Out(X[6]));
59 Mux Mux_inst18(.A(W[5]) ,.B(W[7]) ,.S(B[1]) ,.Out(X[7]));
60 Mux Mux_inst19(.A(W[6]) ,.B(W[8]) ,.S(B[1]) ,.Out(X[8]));
61 Mux Mux_inst1A(.A(W[7]) ,.B(W[9]) ,.S(B[1]) ,.Out(X[9]));
62 Mux Mux_inst1B(.A(W[8]) ,.B(W[10]) ,.S(B[1]) ,.Out(X[10]));
63
64 //B0
65 Mux Mux_inst1C(.A(1'b0) ,.B(X[0]) ,.S(B[0]) ,.Out(T[0]));
66 Mux Mux_inst1D(.A(X[0]) ,.B(X[1]) ,.S(B[0]) ,.Out(T[1]));
67 Mux Mux_inst1E(.A(X[1]) ,.B(X[2]) ,.S(B[0]) ,.Out(T[2]));
68 Mux Mux_inst1F(.A(X[2]) ,.B(X[3]) ,.S(B[0]) ,.Out(T[3]));
69 Mux Mux_inst100(.A(X[3]) ,.B(X[4]) ,.S(B[0]) ,.Out(T[4]));
70 Mux Mux_inst101(.A(X[4]) ,.B(X[5]) ,.S(B[0]) ,.Out(T[5]));
71 Mux Mux_inst102(.A(X[5]) ,.B(X[6]) ,.S(B[0]) ,.Out(T[6]));
72 Mux Mux_inst103(.A(X[6]) ,.B(X[7]) ,.S(B[0]) ,.Out(T[7]));
73 Mux Mux_inst104(.A(X[7]) ,.B(X[8]) ,.S(B[0]) ,.Out(T[8]));
74 Mux Mux_inst105(.A(X[8]) ,.B(X[9]) ,.S(B[0]) ,.Out(T[9]));
75 Mux Mux_inst106(.A(X[9]) ,.B(X[10]) ,.S(B[0]) ,.Out(T[10]));
76
77 assign Y = T[9:0];
78
79 endmodule

```

*Right Barrel Shifter, 5bit Mux, 10bit Mux and Modular Exponent Subtractor are the same as the one's used in HFPFAdder with the code presented above

```

1 //Subtractor
2 module Subtractor
3 (
4     input [10:0] A, B,
5     input cin,
6     output cout,
7     output [10:0] R
8 );
9
10 wire [11:0] C;
11 assign C[0] = cin;
12 assign cout = C[11];
13 FullAdder FullAdder_inst0(.ai(A[0]) ,.bi(B[0]^cin) ,.cini(C[0]) ,.si(R[0]) ,.couti(C[1]));
14 FullAdder FullAdder_inst1(.ai(A[1]) ,.bi(B[1]^cin) ,.cini(C[1]) ,.si(R[1]) ,.couti(C[2]));
15 FullAdder FullAdder_inst2(.ai(A[2]) ,.bi(B[2]^cin) ,.cini(C[2]) ,.si(R[2]) ,.couti(C[3]));
16 FullAdder FullAdder_inst3(.ai(A[3]) ,.bi(B[3]^cin) ,.cini(C[3]) ,.si(R[3]) ,.couti(C[4]));
17 FullAdder FullAdder_inst4(.ai(A[4]) ,.bi(B[4]^cin) ,.cini(C[4]) ,.si(R[4]) ,.couti(C[5]));
18 FullAdder FullAdder_inst5(.ai(A[5]) ,.bi(B[5]^cin) ,.cini(C[5]) ,.si(R[5]) ,.couti(C[6]));
19 FullAdder FullAdder_inst6(.ai(A[6]) ,.bi(B[6]^cin) ,.cini(C[6]) ,.si(R[6]) ,.couti(C[7]));
20 FullAdder FullAdder_inst7(.ai(A[7]) ,.bi(B[7]^cin) ,.cini(C[7]) ,.si(R[7]) ,.couti(C[8]));
21 FullAdder FullAdder_inst8(.ai(A[8]) ,.bi(B[8]^cin) ,.cini(C[8]) ,.si(R[8]) ,.couti(C[9]));
22 FullAdder FullAdder_inst9(.ai(A[9]) ,.bi(B[9]^cin) ,.cini(C[9]) ,.si(R[9]) ,.couti(C[10]));
23 FullAdder FullAdder_instA(.ai(A[10]) ,.bi(B[10]^cin) ,.cini(C[10]) ,.si(R[10]) ,.couti(C[11]));
24
25 endmodule

```

```

1  // Multi 7 Segment display
2  module Multi7segdisplay
3  (
4      input [3:0] HEX0, HEX1, HEX2, HEX3,
5      input CLK, Reset, Load,
6      output logic [0:6] SEG,
7      output logic [3:0] CAT
8  );
9
10     logic [3:0] D0,D1,D2,D3;
11     logic [3:0] Y;
12     logic [1:0] SEL;
13
14     Controller Controller_inst
15     (
16         .MuxRate(CLK) ,    // input MuxRate_sig
17         .Reset(Reset) ,    // input Reset_sig
18         .SEL(SEL) , // output [1:0] SEL_sig
19         .CAT(CAT) // output [3:0] CAT_sig
20     );
21
22     PIPO HEX0_inst
23     (
24         .D(HEX0) , // input [3:0] D_sig
25         .CLK(Load) , // input CLK_sig
26         .CLR(Reset) , // input CLR_sig
27         .Q(D0) // output [3:0] Q_sig
28     );
29
30
31     PIPO HEX1_inst
32     (
33         .D(HEX1) , // input [3:0] D_sig
34         .CLK(Load) , // input CLK_sig
35         .CLR(Reset) , // input CLR_sig
36         .Q(D1) // output [3:0] Q_sig
37     );
38
39     PIPO HEX2_inst
40     (
41         .D(HEX2) , // input [3:0] D_sig
42         .CLK(Load) , // input CLK_sig
43         .CLR(Reset) , // input CLR_sig
44         .Q(D2) // output [3:0] Q_sig
45     );
46
47     PIPO HEX3_inst
48     (
49         .D(HEX3) , // input [3:0] D_sig
50         .CLK(Load) , // input CLK_sig
51         .CLR(Reset) , // input CLR_sig
52         .Q(D3) // output [3:0] Q_sig
53     );

```

```

55     four2one four2one_inst
56     (
57         .SEL(SEL) , // input [1:0] SEL_sig
58         .D0(D0) , // input [3:0] D0_sig
59         .D1(D1) , // input [3:0] D1_sig
60         .D2(D2) , // input [3:0] D2_sig
61         .D3(D3) , // input [3:0] D3_sig
62         .Y(Y) // output [3:0] Y_sig
63     );
64
65     HEX2Seven HEX2Seven_inst
66     (
67         .value(Y) , // input [3:0] value_sig
68         .seg(SEG) // output [0:6] seg_sig
69     );
70
71 endmodule

```

```

1 //Controller FSM
2 module Controller
3 (
4     input MuxRate, Reset,
5     output reg [1:0] SEL,
6     output reg [3:0] CAT
7 );
8     reg [1:0] state, nextstate;
9
10    always @ (negedge MuxRate, negedge Reset)
11        if (Reset == 0) state <= 2'b0; else state <= nextstate;
12
13    always @ (state)
14        case({state})
15            2'b00:begin nextstate = 2'b01; SEL = 2'b00; CAT = 4'b1000; end
16            2'b01:begin nextstate = 2'b10; SEL = 2'b01; CAT = 4'b0100; end
17            2'b10:begin nextstate = 2'b11; SEL = 2'b10; CAT = 4'b0010; end
18            2'b11:begin nextstate = 2'b00; SEL = 2'b11; CAT = 4'b0001; end
19        endcase
20 endmodule

```

```

1 //PIPO register
2 module PIPO
3 (
4     input [3:0] D,
5     input CLK,CLR,
6     output logic [3:0] Q
7 );
8     always_ff @ (posedge CLK, negedge CLR)
9     begin
10         if(CLR==1'b0) Q <= 0;
11         else if(CLK==1'b1) Q <= D;
12     end
13 endmodule

```

```

1 //Hex to Seven segment decoder
2 module HEX2Seven (
3     input [3:0] value,
4     output logic [0:6] seg);
5     always_comb
6     case(value)
7         4'b0000: seg = 7'b1111110; //0
8         4'b0001: seg = 7'b0110000; //1
9         4'b0010: seg = 7'b1101101; //2
10        4'b0011: seg = 7'b1111001; //3
11        4'b0100: seg = 7'b0110011; //4
12        4'b0101: seg = 7'b1011011; //5
13        4'b0110: seg = 7'b1011111; //6
14        4'b0111: seg = 7'b1110000; //7
15        4'b1000: seg = 7'b1111111; //8
16        4'b1001: seg = 7'b1110011; //9
17        4'b1010: seg = 7'b1110111; //A
18        4'b1011: seg = 7'b0011111; //b
19        4'b1100: seg = 7'b1001110; //C
20        4'b1101: seg = 7'b0111101; //d
21        4'b1110: seg = 7'b1001111; //E
22        4'b1111: seg = 7'b1000111; //F
23        default: seg = 7'b0000001; //- for Error
24    endcase
25 endmodule

```

```

1 // Four to one mux
2 module four2one
3 (
4     input [1:0] SEL,
5     input [3:0] D0,D1,D2,D3,
6     output logic [3:0] Y
7 );
8     always_comb
9     case(SEL)
10        2'b00: Y = D0;
11        2'b01: Y = D1;
12        2'b10: Y = D2;
13        2'b11: Y = D3;
14    endcase
15 endmodule
16

```

```

1 //Keypad Input module
2 module keypad_input // Depends: keypad_base(clock_div,keypad_fsm, keypad_decoder), shift_reg
3 #(parameter DIGITS = 4)
4 (
5     input clk,
6     input reset,
7     input [3:0] row,
8     output [3:0] col,
9     output [(DIGITS*4)-1:0] out,
10    // Debug
11    output [3:0] value,
12    output trig
13 );
14 keypad_base keypad_base(
15     .clk(clk),
16     .row(row),
17     .col(col),
18     .value(value),
19     .valid(trig)
20 );
21 shift_reg #(COUNT(DIGITS)) shift_reg(
22     .trig(trig),
23     .in(value),
24     .out(out),
25     .reset(reset)
26 );
27 endmodule

```



```

1 //KeyPad Base Module
2 module keypad_base( // Depends: clock_div, keypad_fsm, keypad_decoder
3     input clk,
4     input [3:0] row,
5     output [3:0] col,
6     output [3:0] value,
7     output valid,
8     // Debug
9     output slow_clock,
10    output sense,
11    output valid_digit,
12    output [3:0] inv_row
13 );
14     assign inv_row = ~row;
15     clock_div #(DIV(100000)) keypad_clock_divider(
16         .clk(clk),
17         .clk_out(slow_clock)
18     );
19     keypad_fsm keypad_fsm(
20         .clk(slow_clock),
21         .row(inv_row),
22         .col(col),
23         .sense(sense)
24     );
25     keypad_decoder #(BASE(16)) keypad_key_decoder(
26         .row(inv_row),
27         .col(col),
28         .value(value),
29         .valid(valid_digit)
30     );
31     assign valid = valid_digit && sense;
32 endmodule

```

```

1 //Clock Divider Module
2 module clock_div
3     #(
4         parameter WIDTH = 32,
5         parameter DIV = 50 // Defaults to 1MHz
6     )
7     (
8         input clk, reset,
9         output clk_out
10    );
11    reg [WIDTH-1:0] r_reg;
12    wire [WIDTH-1:0] r_nxt;
13    reg clk_track;
14    always @(posedge clk or posedge reset)
15    begin
16        if (reset)
17        begin
18            r_reg <= 0;
19            clk_track <= 1'b0;
20        end
21        else if (r_nxt == DIV)
22        begin
23            r_reg <= 0;
24            clk_track <= ~clk_track;
25        end
26        else
27            r_reg <= r_nxt;
28        end
29        assign r_nxt = r_reg+1;
30        assign clk_out = clk_track;
31    endmodule

```

```

1 //Keypad FSM module
2 module keypad_fsm(
3     input clk,
4     input [3:0] row,
5     output reg [3:0] col,
6     output sense,
7     // Debug
8     output reg [3:0] state,
9     output trig
10 );
11 assign trig = row[0] || row[1] || row[2] || row[3];
12 assign sense = state == 10;
13 always @ (posedge clk)
14 begin
15     case (state)
16     0: begin col = 4'b1111; state = 1; end
17     1: if (trig) begin state = 2; end
18     2: begin col = 4'b0001; state = 3; end
19     3: if (trig) begin state = 10; end else begin state = 4; end
20     4: begin col = 4'b0010; state = 5; end
21     5: if (trig) begin state = 10; end else begin state = 6; end
22     6: begin col = 4'b0100; state = 7; end
23     7: if (trig) begin state = 10; end else begin state = 8; end
24     8: begin col = 4'b1000; state = 9; end
25     9: if (trig) begin state = 10; end else begin state = 0; end
26     10: begin state = 11; end
27     11: if (~trig) begin state = 0; end
28     endcase
29 end
30 endmodule

```

```

1 //Keypad Decoder module
2 module keypad_decoder
3 #(
4     parameter BASE = 16 // Default Base 10 (Options: 10,16)
5 )
6 (
7     input [3:0] row,
8     input [3:0] col,
9     output reg [3:0] value,
10    output reg valid // Optional
11 );
12 always @ (row, col)
13 begin
14     if (BASE == 10)
15     begin
16         // 1 2 3 A
17         // 4 5 6 B
18         // 7 8 9 C
19         // E 0 F D
20         case ({row, col})
21         8'b0001_0001: begin value = 1; valid = 1; end // 1
22         8'b0001_0010: begin value = 2; valid = 1; end // 2
23         8'b0001_0100: begin value = 3; valid = 1; end // 3
24         8'b0001_1000: begin value = 10; valid = 1; end // A
25         8'b0010_0001: begin value = 4; valid = 1; end // 4
26         8'b0010_0010: begin value = 5; valid = 1; end // 5
27         8'b0010_0100: begin value = 6; valid = 1; end // 6
28         8'b0010_1000: begin value = 11; valid = 1; end // B
29         8'b0100_0001: begin value = 7; valid = 1; end // 7
30         8'b0100_0010: begin value = 8; valid = 1; end // 8
31         8'b0100_0100: begin value = 9; valid = 1; end // 9
32         8'b0100_1000: begin value = 12; valid = 1; end // C
33         8'b1000_0001: begin value = 14; valid = 1; end // E
34         8'b1000_0010: begin value = 0; valid = 1; end // 0
35         8'b1000_0100: begin value = 15; valid = 1; end // F
36         8'b1000_1000: begin value = 13; valid = 1; end // D
37         default: begin value = 0; valid = 0; end // Misc
38     endcase
39 end

```

```

37         default: begin value = 0; valid = 0; end // Misc
38     endcase
39 end
40 else if (BASE == 16)
41     begin
42         // 0 1 2 3
43         // 4 5 6 7
44         // 8 9 A B
45         // C D E F
46         case ({row, col})
47             8'b0001_0001: begin value = 0; valid = 1; end // 0
48             8'b0001_0010: begin value = 1; valid = 1; end // 1
49             8'b0001_0100: begin value = 2; valid = 1; end // 2
50             8'b0001_1000: begin value = 3; valid = 1; end // 3
51             8'b0010_0001: begin value = 4; valid = 1; end // 4
52             8'b0010_0010: begin value = 5; valid = 1; end // 5
53             8'b0010_0100: begin value = 6; valid = 1; end // 6
54             8'b0010_1000: begin value = 7; valid = 1; end // 7
55             8'b0100_0001: begin value = 8; valid = 1; end // 8
56             8'b0100_0010: begin value = 9; valid = 1; end // 9
57             8'b0100_0100: begin value = 10; valid = 1; end // A
58             8'b0100_1000: begin value = 11; valid = 1; end // B
59             8'b1000_0001: begin value = 12; valid = 1; end // C
60             8'b1000_0010: begin value = 13; valid = 1; end // D
61             8'b1000_0100: begin value = 14; valid = 1; end // E
62             8'b1000_1000: begin value = 15; valid = 1; end // F
63         default: begin value = 0; valid = 0; end // Misc
64     endcase
65 end
66 else
67     begin
68         value = 0; valid = 0; // Invalid Base
69     end
70 end
71 endmodule

```

```

1 //Shift Register Module
2 module shift_reg
3     #(
4         parameter COUNT = 4,
5         parameter WIDTH = 4
6     )
7     (
8         input trig, reset, dir, // Left = 0, Right = 1
9         input [WIDTH-1:0] in,
10        output reg [(COUNT*WIDTH)-1:0] out
11    );
12    always @ (posedge trig, negedge reset)
13    begin
14        if (~reset)
15            out <= 0;
16        else
17            begin
18                if (dir)
19                    begin // 1 = Right
20                        out <= out >> WIDTH;
21                        out[(COUNT*WIDTH)-1:((COUNT*WIDTH)-1)-WIDTH] <= in;
22                    end
23                else
24                    begin // 0 = Left
25                        out <= out << WIDTH;
26                        out[WIDTH-1:0] <= in;
27                    end
28            end
29    end
30 endmodule

```